

INSTRUMENTATION WORKSHOP LUNABOTICS 2026

DANIEL BARREIRO TORRES
SOFTWARE TEAM LEADER



INTER BAYAMÓN


AGENDA

- **Circuit terminology**
- **Multimeters & measurements**
- **Wiring loads**
- **Bench PSU basics**
- **Hands on deliverable**

CIRCUIT TERMINOLOGY



CIRCUIT TERMINOLOGY

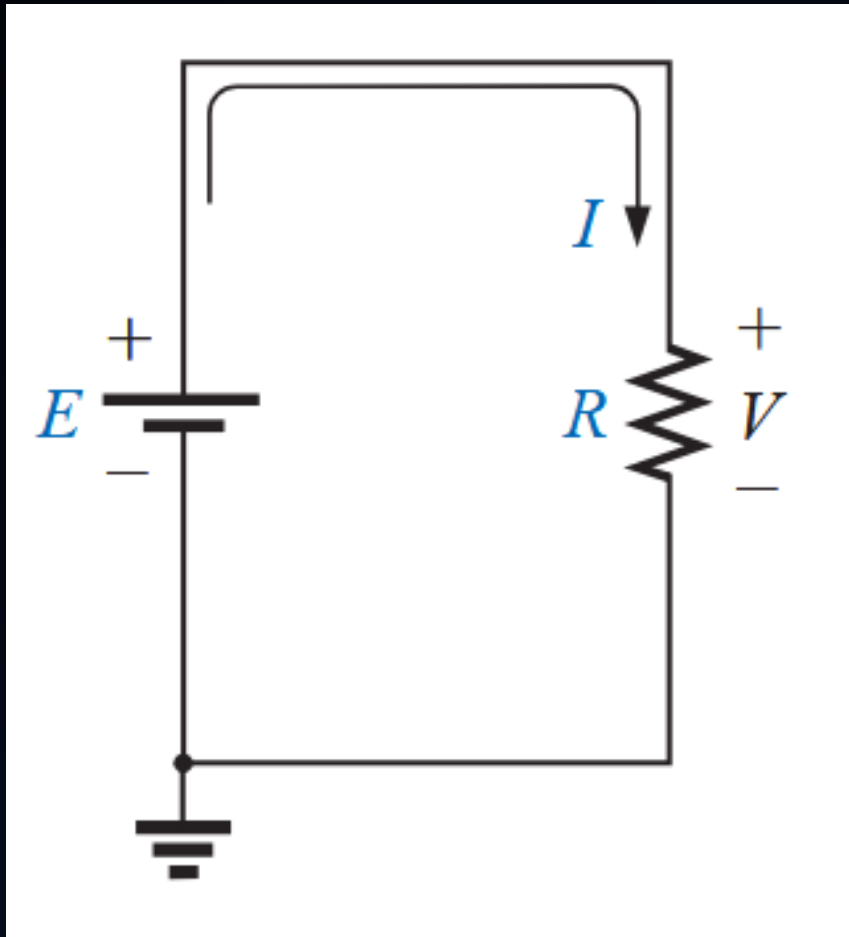

A circuit is a closed path where current can flow; it is essential to be familiar with schematic symbols and terminology to advance in our project


OHMS LAW

V = Voltage (volts)

R = Resistance (ohms)

I = Current (Amperes)



$$V=RI$$

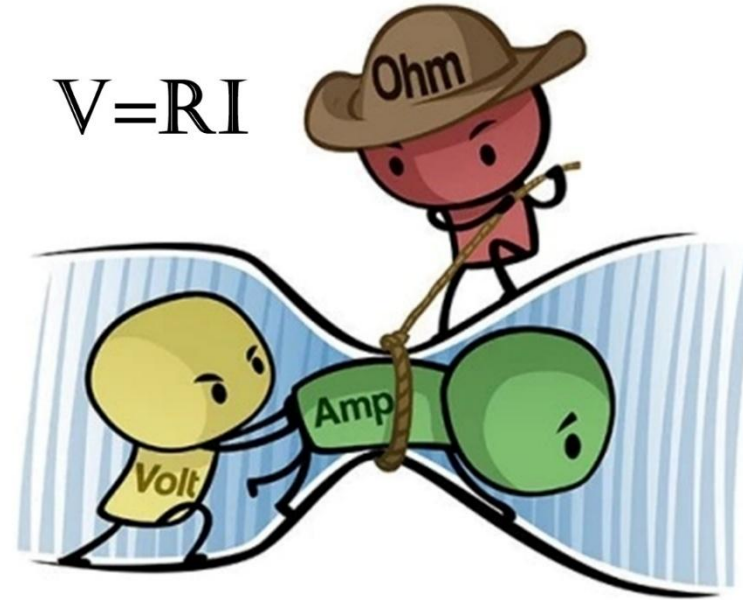






SERIES & PARALLEL CIRCUITS

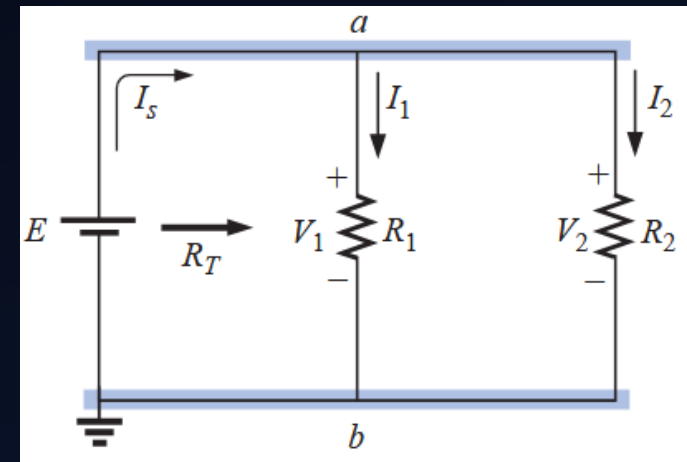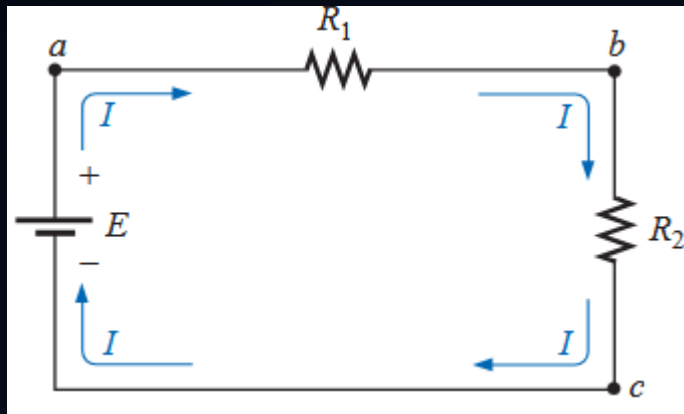- In a series circuit, the current is the same across all elements but voltage drops across elements
- Parallel circuits all elements have the same voltage but the current divides between them



A FAMILIAR IMAGE...

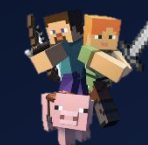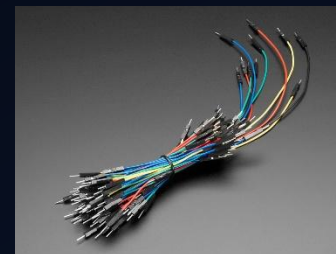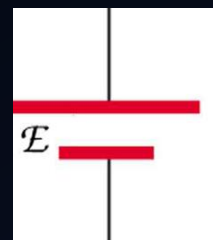


A FAMILIAR IMAGE...


Series circuits have the same current, but voltage drops across loads

- Voltage diminishes as more loads are added in series
- Same current through all loads




A FAMILIAR IMAGE...

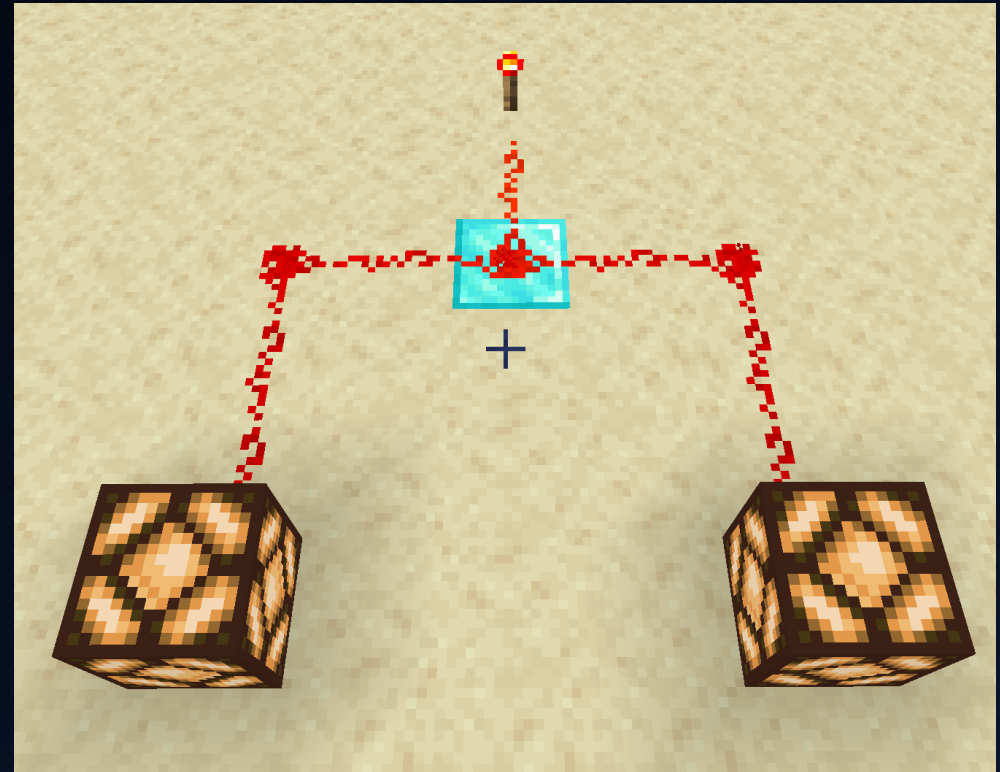- Parallel circuits have the same voltage for all loads sharing a node
- At the node  the current divides between the lamps



OPEN & CLOSED CIRCUITS

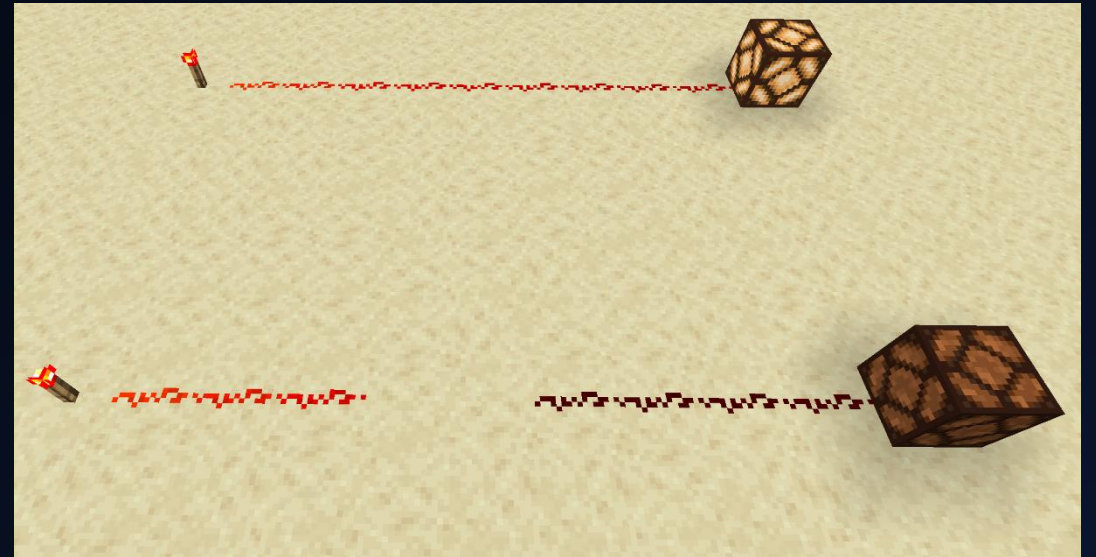- In a closed circuit, current passes uninterrupted
- In an open circuit, no current can pass



DIGITAL MULTIMETER (DMM)


WHY USE A DMM?

“Measure twice, cut once.”

- As engineers, it is good practice to always measure
- In our case electronic components are measured with the DMM



HOW TO USE A DMM?: VOLTAGE MEASUREMENTS

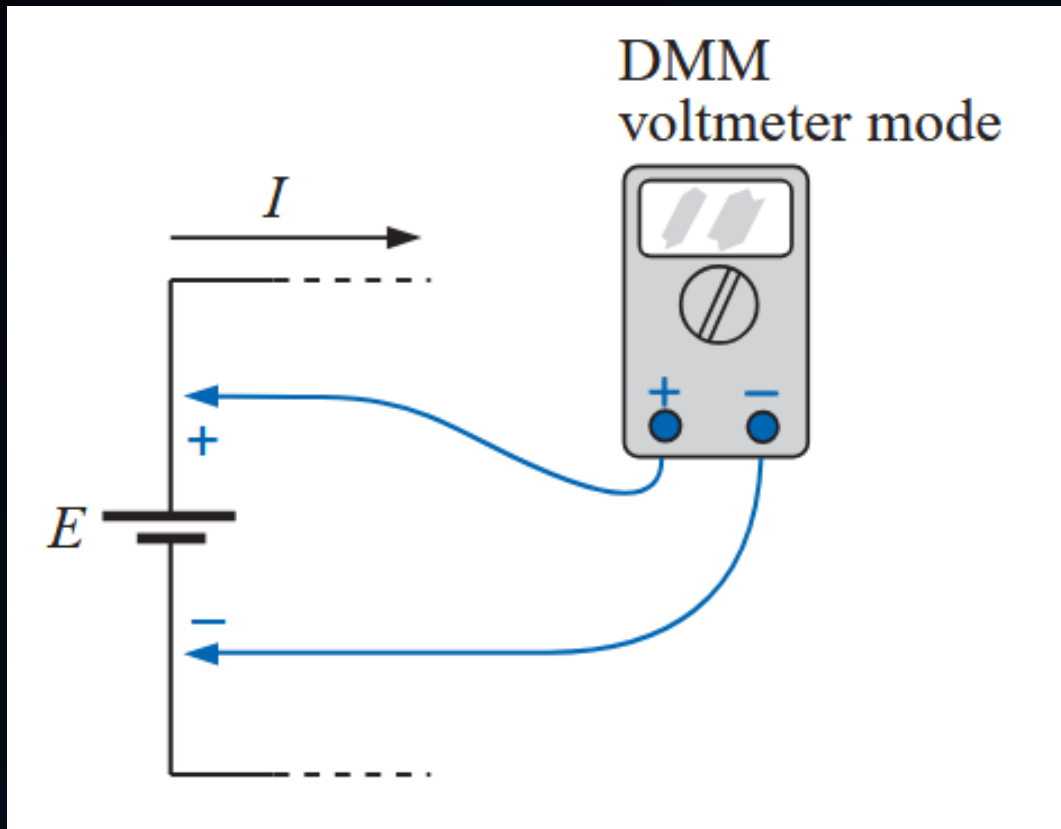

To measure the potential difference across two points, place the leads in parallel to that element

- Note: A negative sign appears in front of the measurement just means the wires are backwards (this is not an issue)


HOW TO USE A DMM?: VOLTAGE MEASUREMENTS

To Measure Voltage

Ranges: 100 mV, 1 V, 10 V, 100 V, 1000 V (750 Vac)

Maximum resolution: 100 nV (on 100 mV range)

AC technique: true RMS, ac-coupled

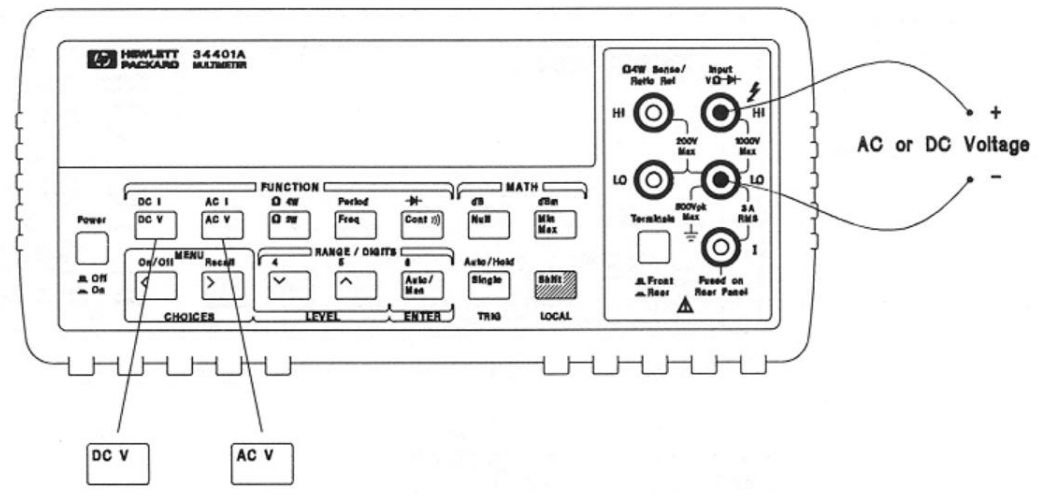


Place the black wire in the LO pin, and red wire in the V input pin

- Select DC V for direct current measurements
- If using the front side terminals, make sure the Terminals button is not pressed down

HOW TO USE A DMM?: CONTINUITY

To verify if two points are connected, put the DMM in continuity mode and probe the two desired points

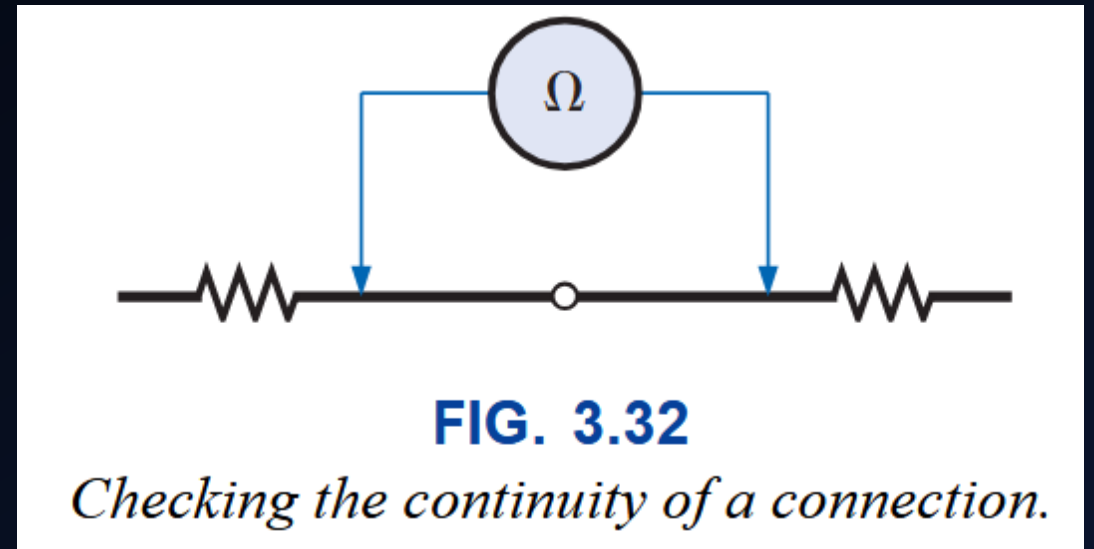
- A 'beep' sound indicates continuity (closed circuit)
- No beep indicates no continuity (open circuit)



HOW TO USE A DMM?: CURRENT MEASUREMENTS

Current is always measured in series

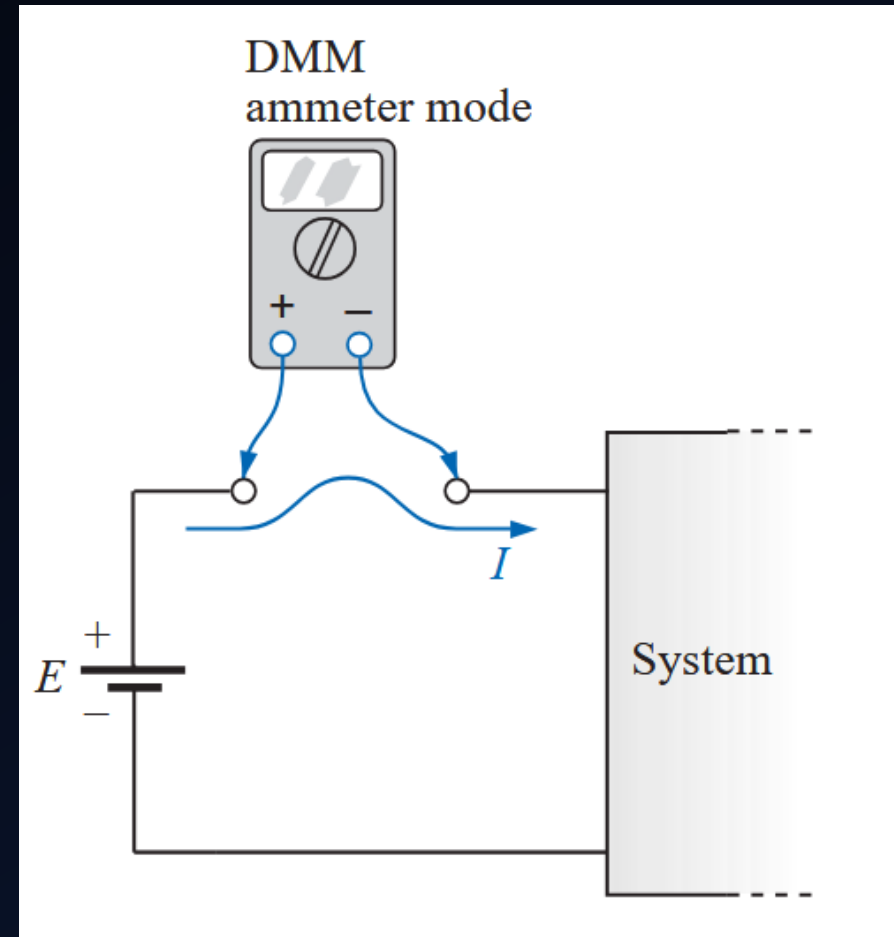
- The low resistance in the Ammeter mode of the DMM completes the circuit without causing disturbance



HOW TO USE A DMM?: CURRENT MEASSUREMENTS

To Measure Current

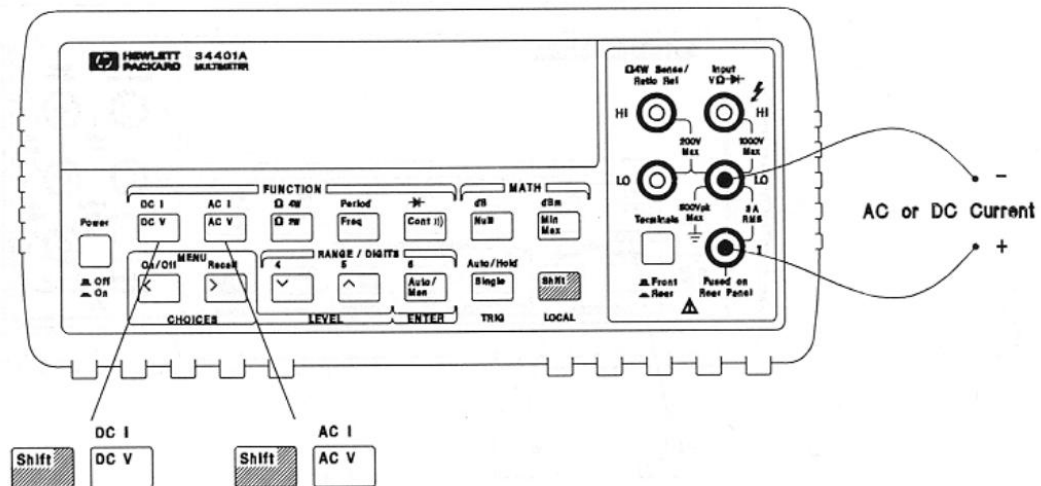Ranges: 10 mA (dc only), 100 mA (dc only), 1 A , 3 A
Maximum resolution: 10 nA (on 10 mA range)
AC technique: true RMS, ac-coupled



- Press the shift key, then DC V
- Place the black lead on the LO terminal, and the red lead on the “Fused on Rear Panel” terminal marked by a capital **I**


DO NOT MEASURE CURRENT IN PARALLEL, DOING SO MAY DAMAGE THE DMM

SO WHAT IF CURRENT IS MEASURED IN PARALLEL?.....




WIRING LOADS

HOW TO USE A BREADBOARD

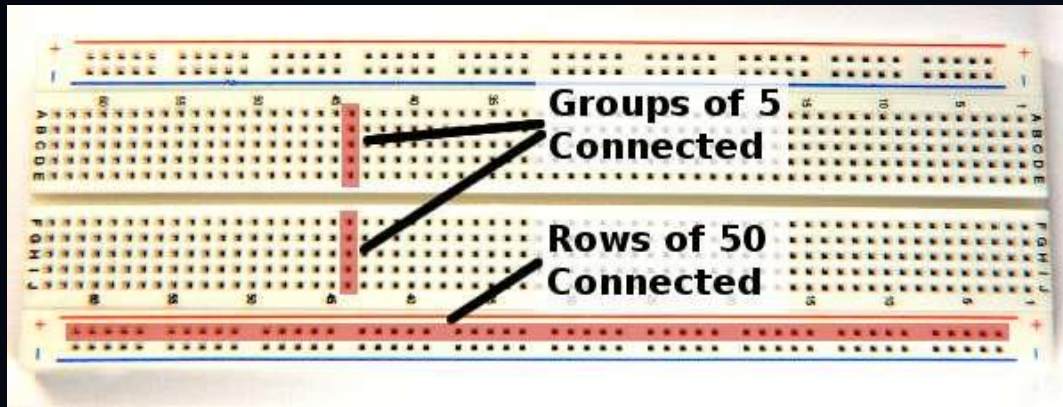

- Numbered rows are connected internally
- + & - Rows serve as a bus, placing one positive and ground wire respectively will power the rails

BANANA WIRES

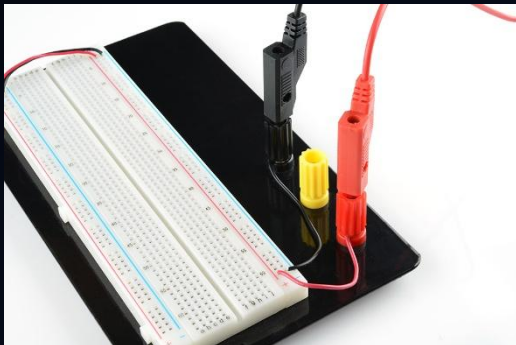


- These wires will come from the PSU into the breadboard
- From the breadboard terminal, jumpers can be added

BENCH PSU & SAFETY


BENCH PSU BASICS

The PSU found at the CUNAR Lab is a current limiting PSU

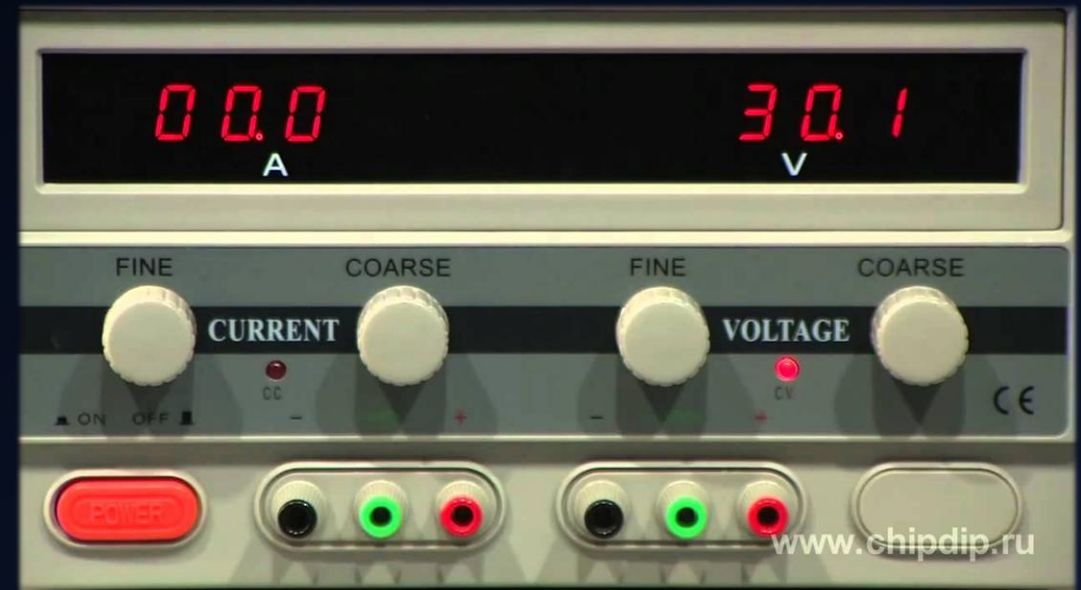- (+) - Positive terminal
- (-) - Negative terminal




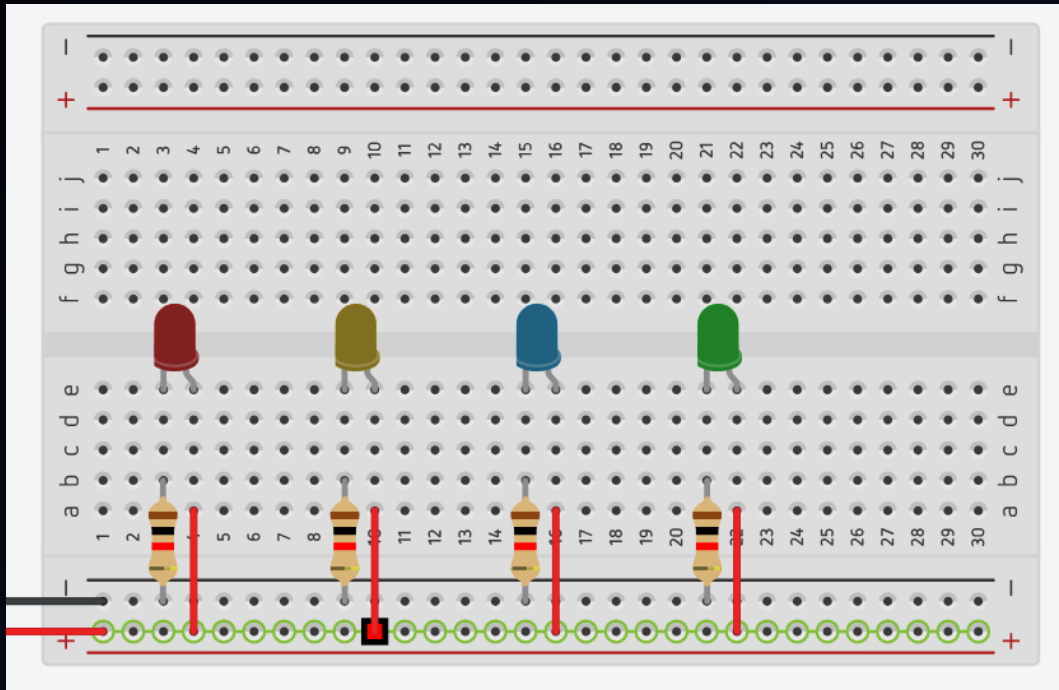Hands on activity #1: Voltage measurement



- Power on the LEDs with the breadboard using four 220 Ω resistors in the arrangement seen in the picture
 - a) Measure the source voltage
 - b) Measure the voltage across each LED

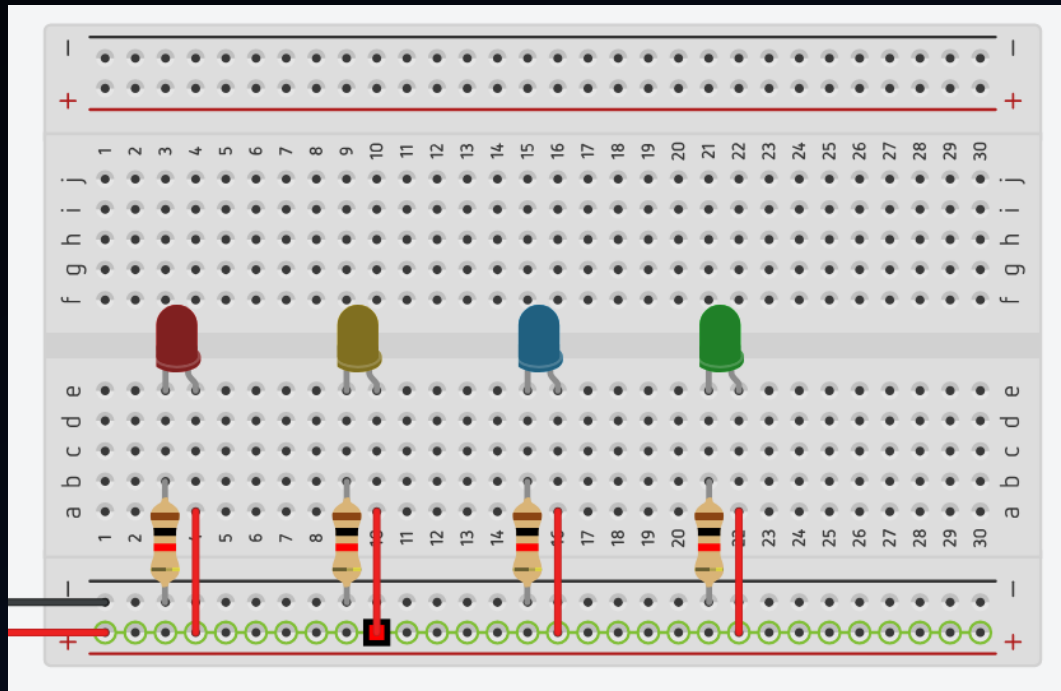Hands on activity #2: Resistance measurement



- Turn off the power supply before measuring
- Measure the voltage drop across each resistor

KEY TAKEAWAYS

- Electricity isn't dangerous, arrogance is
- Set PSU voltage and current knob all the way to the left before powering on (0v and 0A)
- Always assume circuits are energized
- Disconnect/Turn off any voltage source when touching the circuit
- If unsure, do not power the circuit. It is good practice to ask your "elders" (no one will nor are supposed to judge you)
- When leaving the lab, turn off equipment and multiplug on the wall
- **DO NOT MEASURE CURRENT IN PARALLEL!!!**